
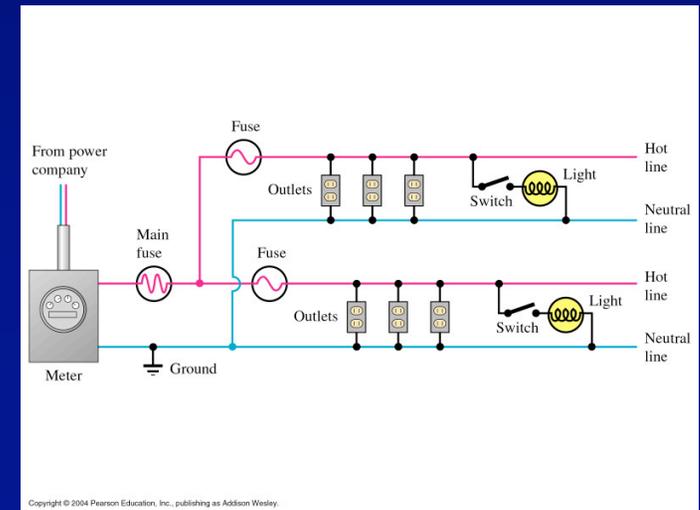
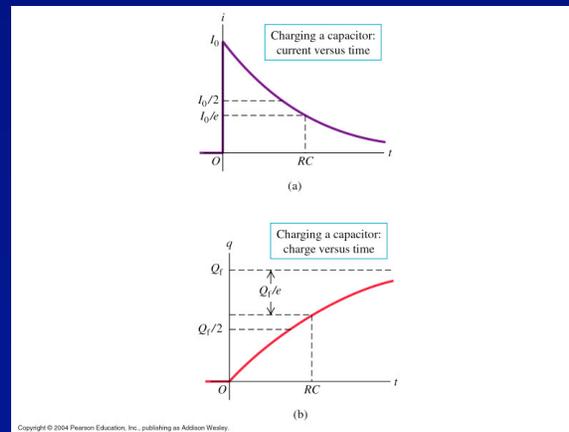

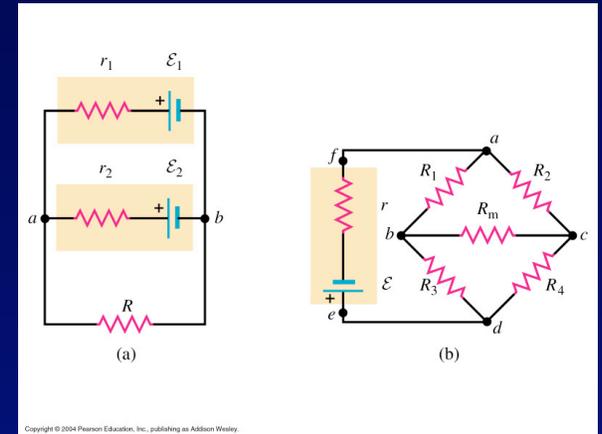
# Chapter 26: Direct-Current Circuits (Part 2)

- Electrical measuring instruments (con'd)
- RC circuits
- Electrical Safety



# **Electrical Measuring Instruments**

***New Topic***

## Example: Impact of Ammeter and Voltmeter on measurements

- Let's do the numbers.
  - ▶ Ammeter reading 0.1 A, resistance  $R_A=2.0 \Omega$ .
  - ▶ Voltmeter reading 12.0 V, resistance  $R_V=10 \text{ k}\Omega$

**Ideal case ( $R_A=0, R_V=\infty$ ):**  
 $R=V/I=12/0.1=120 \Omega$


**Case (a):** voltage across R is less than 12V.

$$R_a=(12-0.1*2.0)/0.1=118 \Omega$$

**Case (b):** Current in R is less than 0.1 A.


$$R_b=12/(0.1-12/10000)=121 \Omega$$

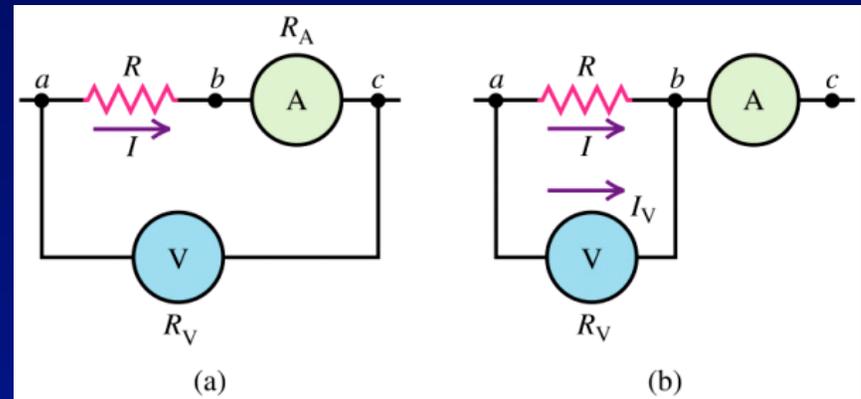Small difference, but must be taken into account in precision measurements.



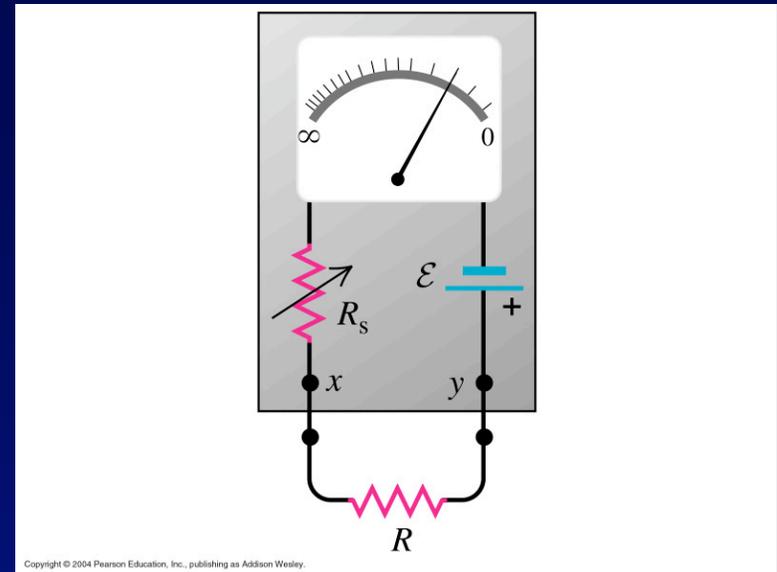
## Ohmmeter

Open between  $x$  and  $y$ , no deflection ( $R=\infty$ ). Short between  $x$  and  $y$ : full-deflection ( $R=0$ ). Any  $R$  in between is read directly.


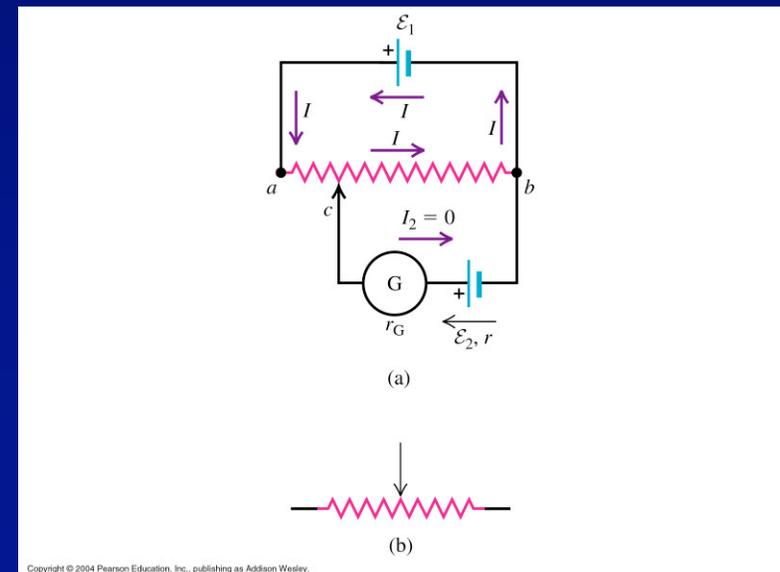
## Potentiometer


A known voltage is balanced by sliding the contact  $c$  until the current through the unknown emf is zero:  $\mathcal{E}_2 = IR_{cb}$



## ConceptTest 26.4
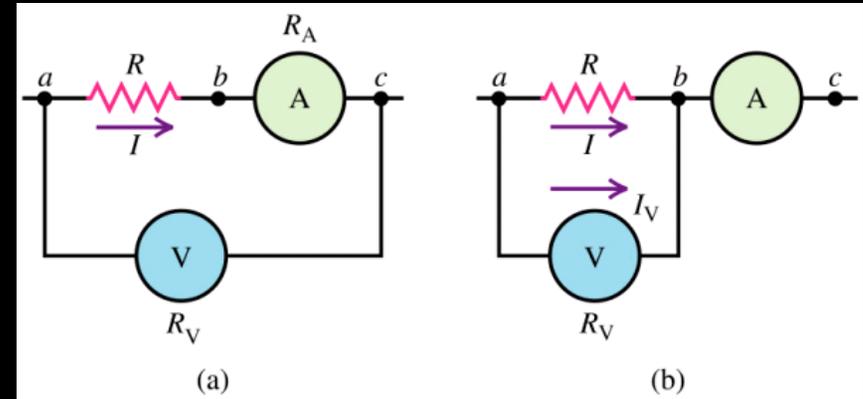
## Ammeter and Voltmeter

- In the two circuits to measure an unknown resistance by  $R=V/I$ , the readings on the A and the V-meters are the same. Taking the resistance of the A and V-meters into account, what can you say about the resistance actually measured in each case?




- 1)  $R_a > R_b$     2)  $R_a < R_b$     3)  $R_a = R_b$

# RC Circuit

*New Topic*
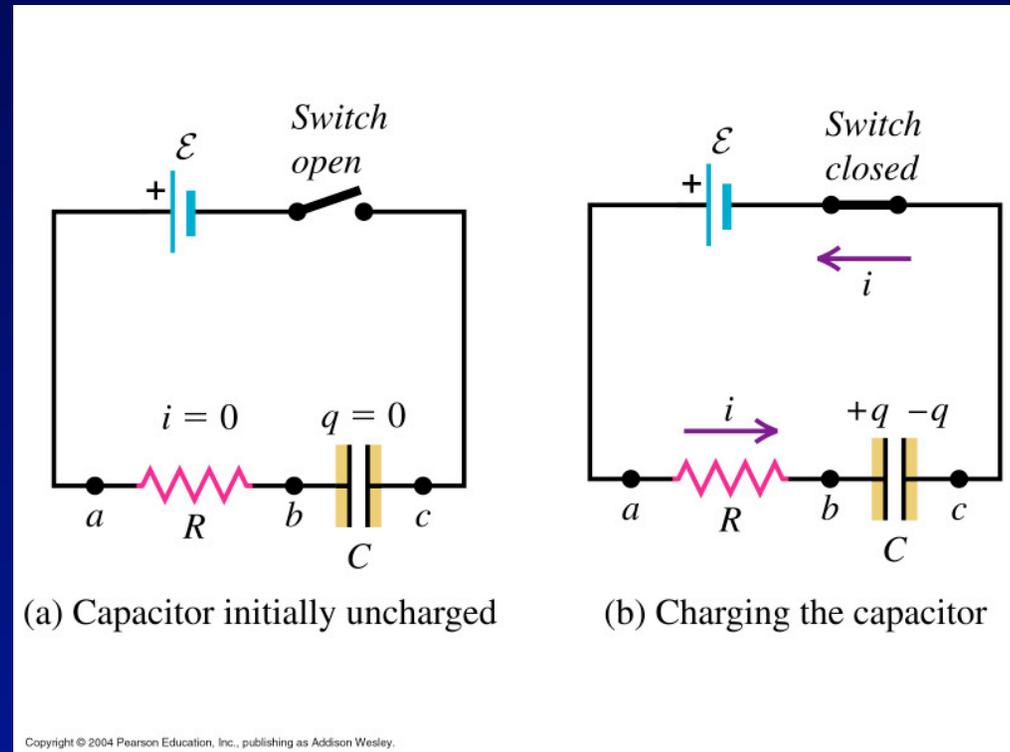
# What happens if we add a capacitor in a DC circuit?

- Consider a **charging** circuit as shown.
- Charge will start to flow to the capacitor.
  - ▶ A current (recall  $i=dq/dt$ ) flows in the circuit
- Voltage across the capacitor will increase
  - ▶ recall  $V=q/C$
- The current decreases, eventually comes to a stop.
- Now the capacitor has maximum charge  $Q=C\mathcal{E}$
- Now everything is quiet.



## How to put it in more precise terms?

# RC Circuit: charging

Apply loop rule:


$$\mathcal{E} - iR - \frac{q}{C} = 0$$

This is a differential equation for  $q$  (with the initial condition  $q=0$  at  $t=0$ ):

$$R \frac{dq}{dt} + \frac{q}{C} - \mathcal{E} = 0$$

Solution:  $q(t) = C\mathcal{E} \left(1 - e^{-t/RC}\right)$
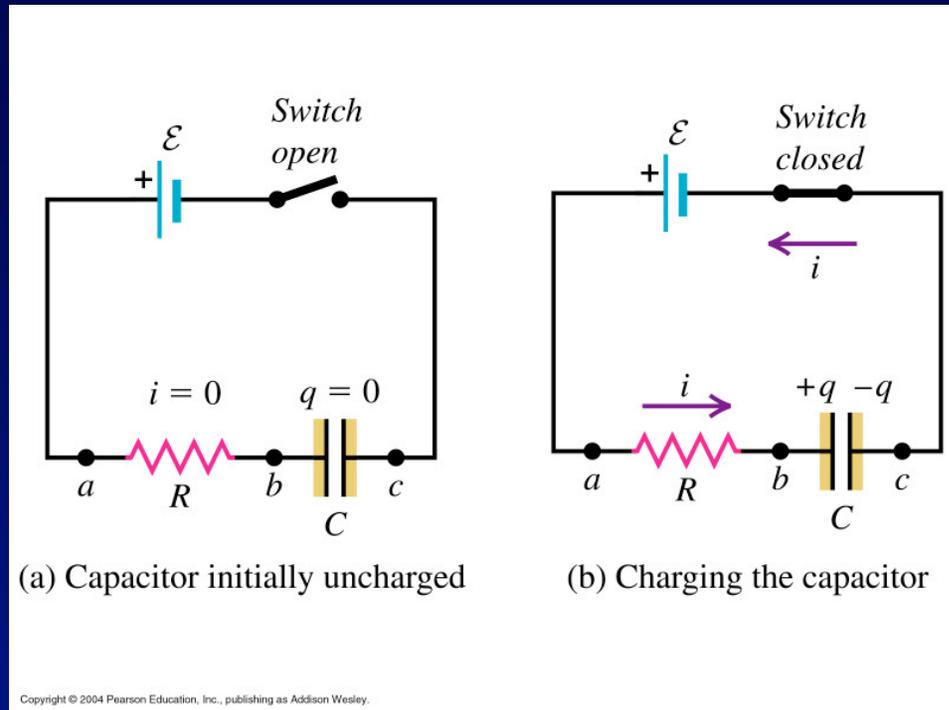
$$i(t) = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$



Conclusion:

- a) Exponential time dependence
- b) Time constant  $RC = \tau$

Example: For  $R=10 \text{ k}\Omega$  and  $C=5 \text{ }\mu\text{F}$ , the time constant is **50 ms**.



# RC Circuit: charging

$$q(t) = C\mathcal{E} \left(1 - e^{-t/RC}\right)$$

At  $t=RC$ , charge increases to 63% of its maximum value.  
(recall  $e=2.713$ )

$$i(t) = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

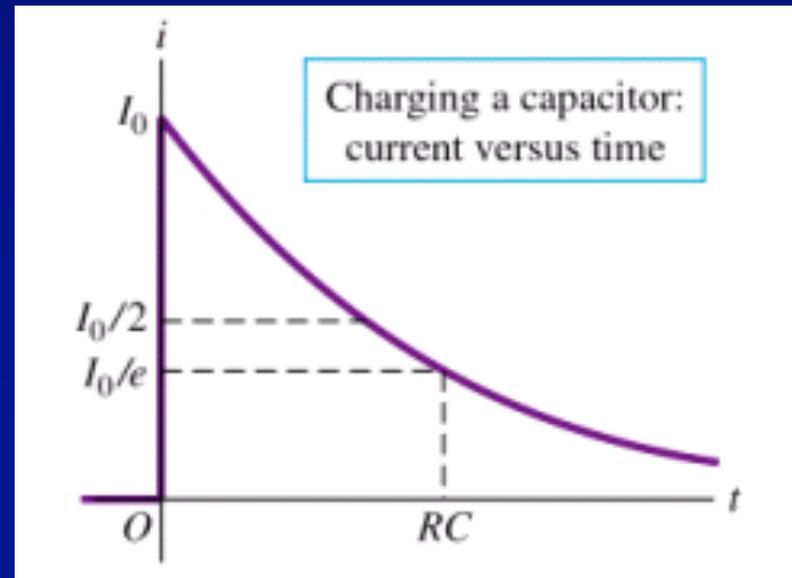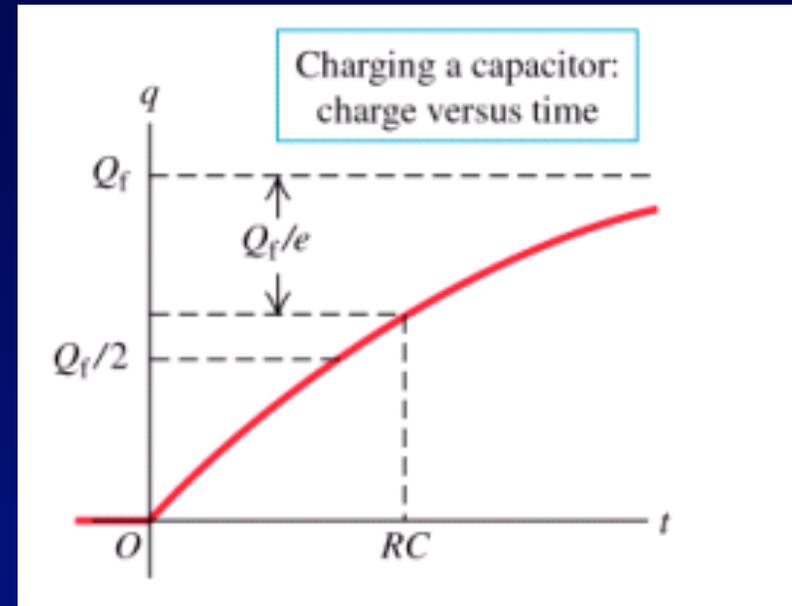At  $t=RC$ , current decreases to 37% of its maximum value.



# RC Circuit: discharging

Apply loop rule:


$$-iR - \frac{q}{C} = 0$$

This is a differential equation for  $q$  (with the initial condition  $q=Q_0$  at  $t=0$ ):

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

Solution:  $q(t) = Q_0 e^{-t/RC}$
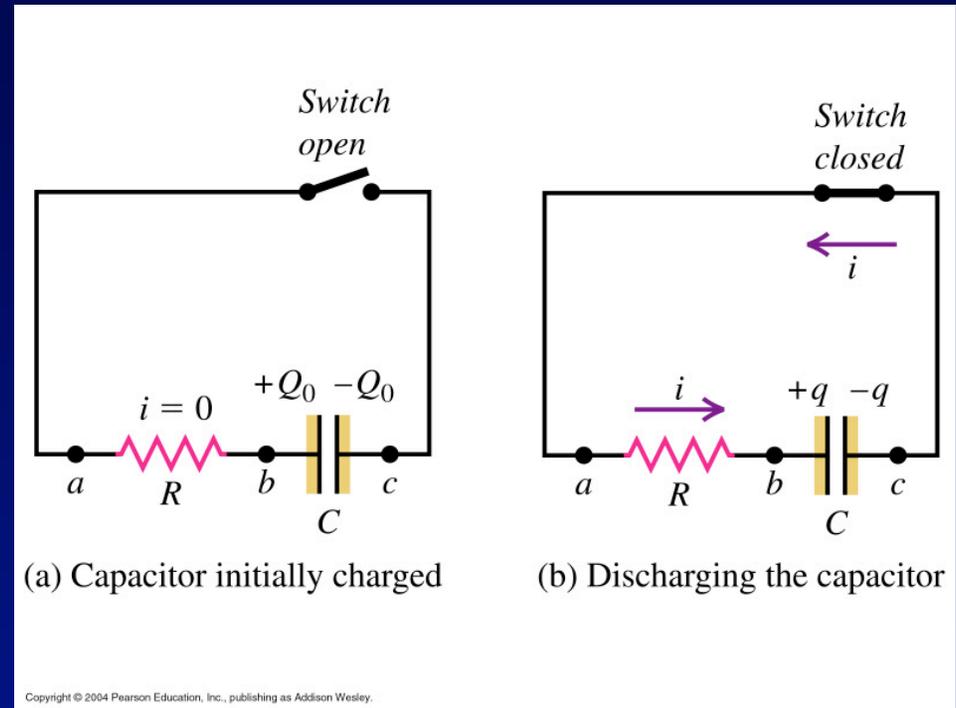
$$i(t) = \frac{dq}{dt} = -\frac{Q_0}{RC} e^{-t/RC}$$



Conclusion:

a) Same exponential time dependence

b) Same time constant  $RC = \tau$



# RC Circuit: discharging

$$q(t) = Q_0 e^{-t/RC}$$

At  $t=RC$ , charge decreases to 37% of its maximum value.


$$i(t) = \frac{dq}{dt} = -\frac{Q_0}{RC} e^{-t/RC}$$

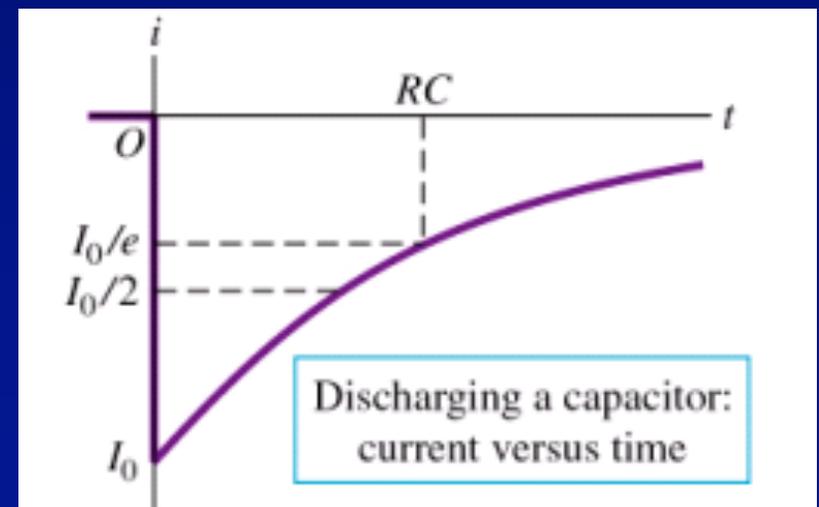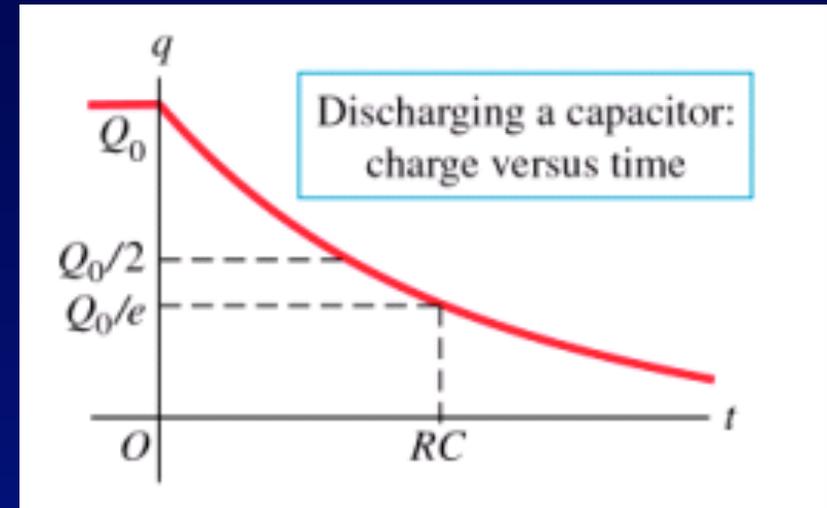At  $t=RC$ , current increases to 37% of its maximum value.




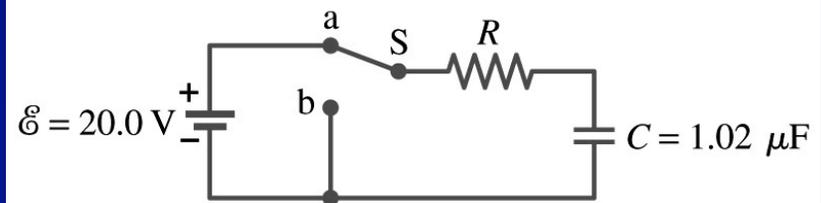
## Example: discharging RC circuit

- In the RC circuit shown, the battery has fully charged the capacitor. Then at  $t=0$ , the switch is thrown from a to b. The current is observed to decrease to  $\frac{1}{2}$  of its initial value in  $40\mu\text{s}$ .
  - What is  $R$ ?
  - What is  $Q$ , the charge on the capacitor, at  $t=0$ ?
  - What is  $Q$  at  $t=60\mu\text{s}$


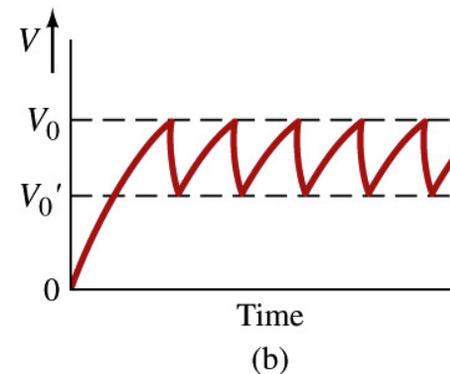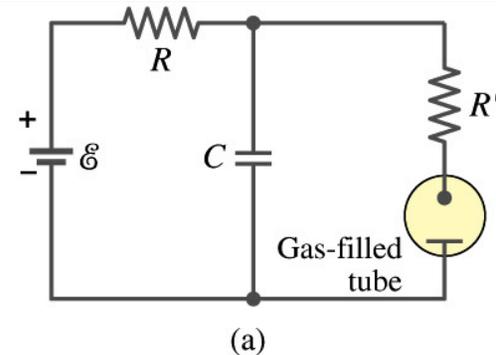
## Application of RC Circuits

- The time dependence and time constant  $\tau=RC$  for charging and discharging provides a means to change voltage with an adjustable frequency: the **sawtooth voltage**
  - automobile turn signal
  - intermittent wiper
  - traffic flashing light
  - heart pacemaker
  - and more




## ConcepTest 26.5

## RC Circuits

- In charging a capacitor, how much total energy (in terms of  $\mathcal{E}$ ,  $R$ ,  $C$ ) is delivered by the battery?

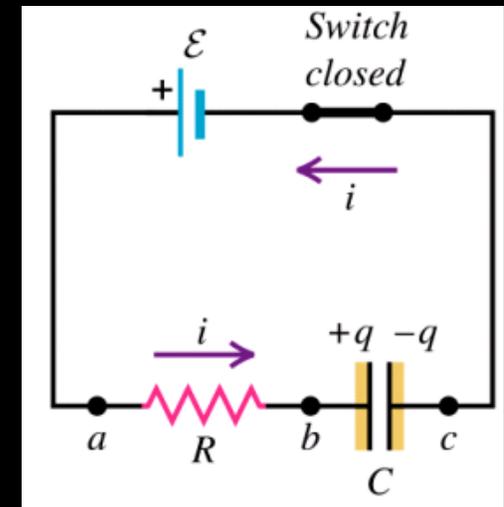
(a)  $\mathcal{E}^2/R$  (b)  $\mathcal{E}^2/(2R)$  (c)  $C\mathcal{E}^2$  (d)  $C\mathcal{E}^2/2$



## ConceptTest 26.6
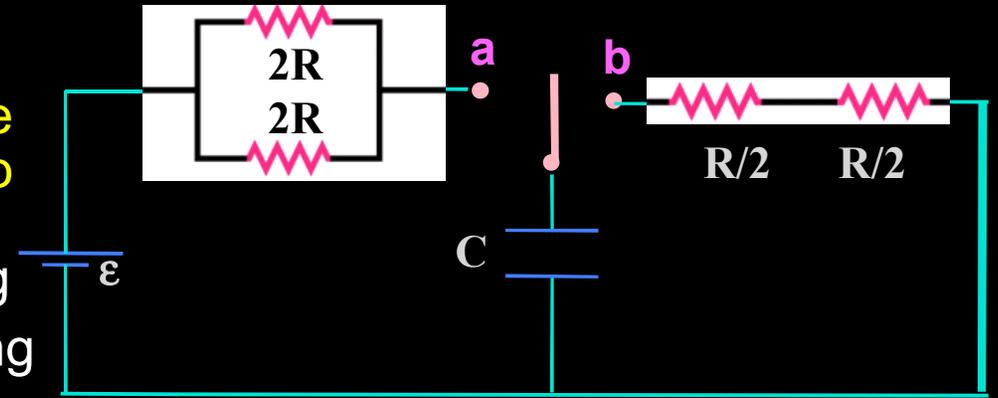
## RC Circuits

- In the circuit shown, the switch is first thrown to position a to charge the capacitor, then to position b to discharge it. What is the relationship between the charging time constant ( $\tau_1$ ) and discharging time constant ( $\tau_2$ ) ?



- (a)  $\tau_1 < \tau_2$    (b)  $\tau_1 = \tau_2$    (c)  $\tau_1 > \tau_2$

# **Electrical Safety**

***New Topic***


# Injuries through Electricity

- If we touch a charged conductor:
  - ▶ potential difference between conductor and ground
  - ▶ your body becomes a part of the circuit for current!
- Extent of injury depends on **current** flow through your body

$$I = \frac{V}{R}$$

*usually 120 V*

*resistance of the body*

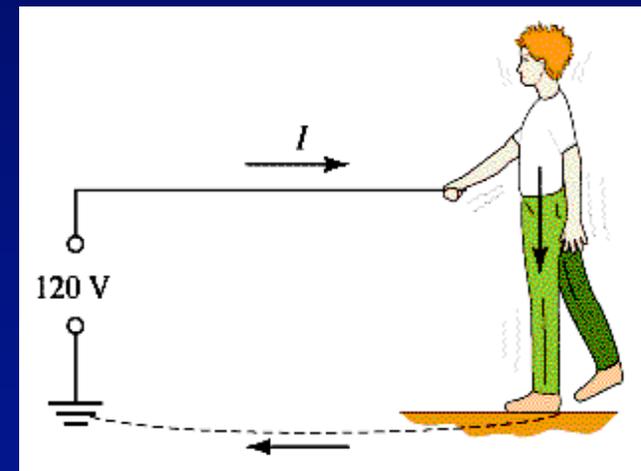

$R = 0.5 \times 10^6 \ \Omega$  (for dry skin)  $\rightarrow$

$I = 0.24 \text{ mA}$


$R = 0.5 \times 10^4 \ \Omega$  (for wet skin)  $\rightarrow$

$I = 24 \text{ mA}$





# Injuries through Electricity

<u>Current</u>	<u>Effect</u>	<u>Fatal?</u>
1 mA	mild shock	no
5 mA	painful	no
10 mA	paralysis of motor muscles	no
20 mA	breathing stops	minutes
100 mA	heart stops	seconds
1000 mA	serious burns	instantly

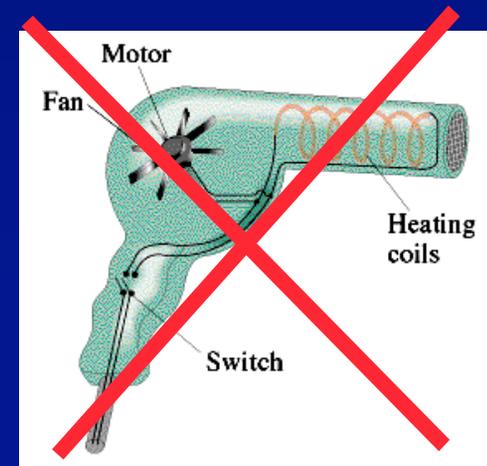***So don't dry your  
hair in the bathtub!***



# Grounding of Devices

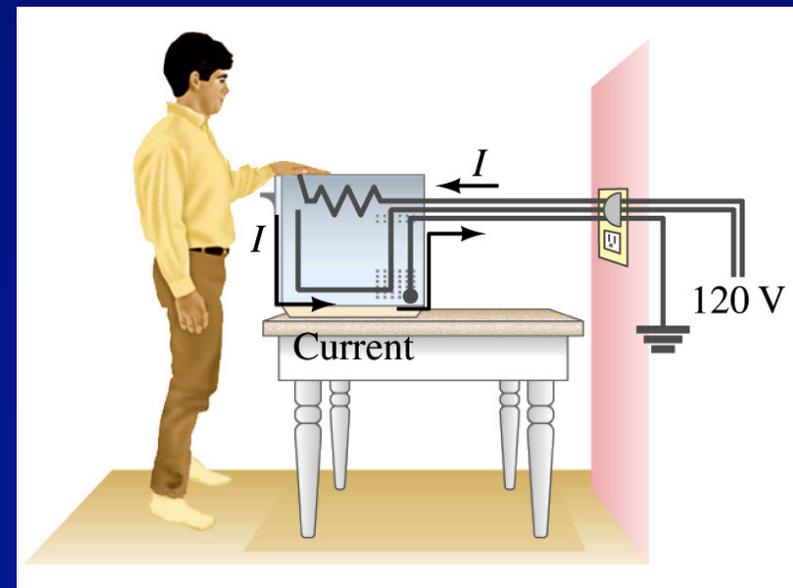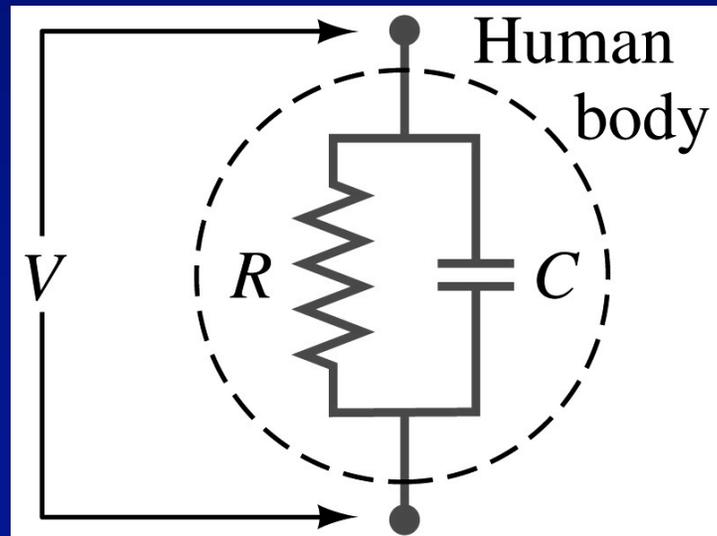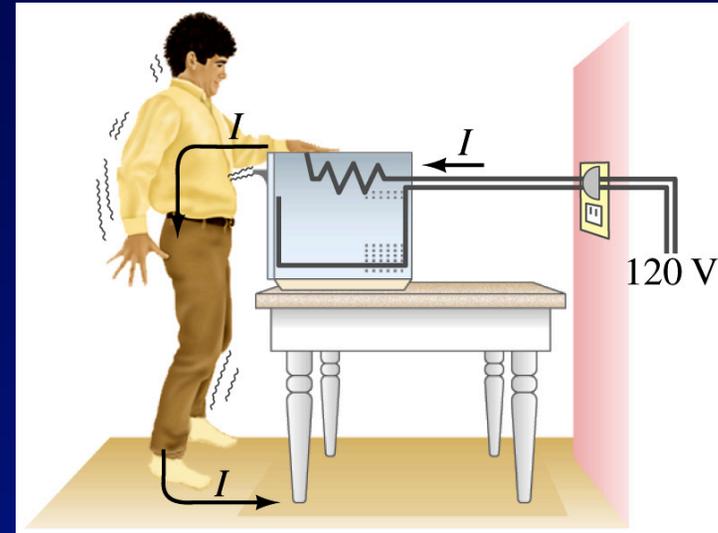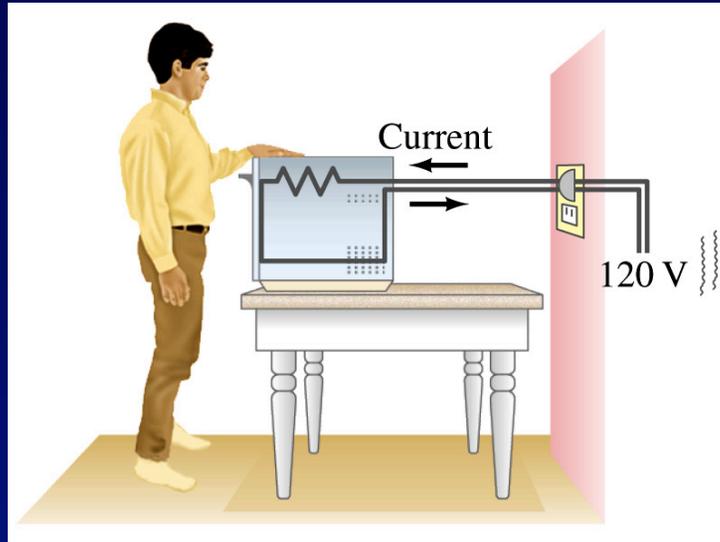


## Artificial Respiration


- A current of around **70 mA** passing through the body for a second or more can cause the heart to beat irregularly (ventricular fibrillation)
  - If it lasts long, death results.
- A much larger current of about **1 A** can bring the heart to a standstill. Upon release of the current, the heart returns to its normal rhythm. This shock may not be a bad thing.
  - **Defibrillator**: a device to restart the heart by applying a high voltage (therefore high current) shock.
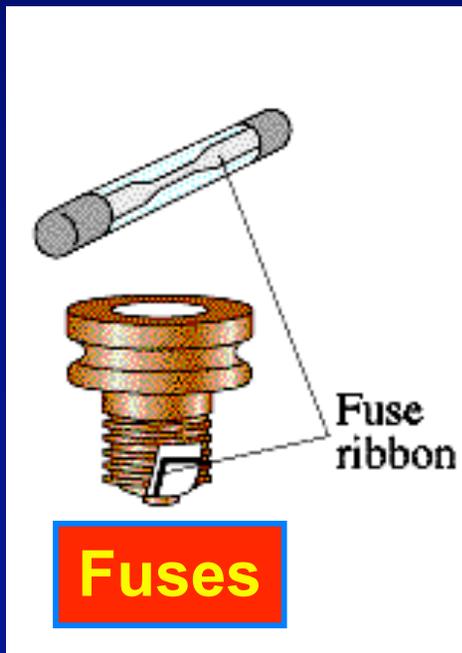
# Fuses and Breakers


- Too many devices in the circuit can require more current than the wires can handle -- overheating of wires is a fire hazard !
- If an electric circuit gets “overloaded” (too much current) fuses or circuit breakers interrupt the flow of current.



## Circuit Breaker

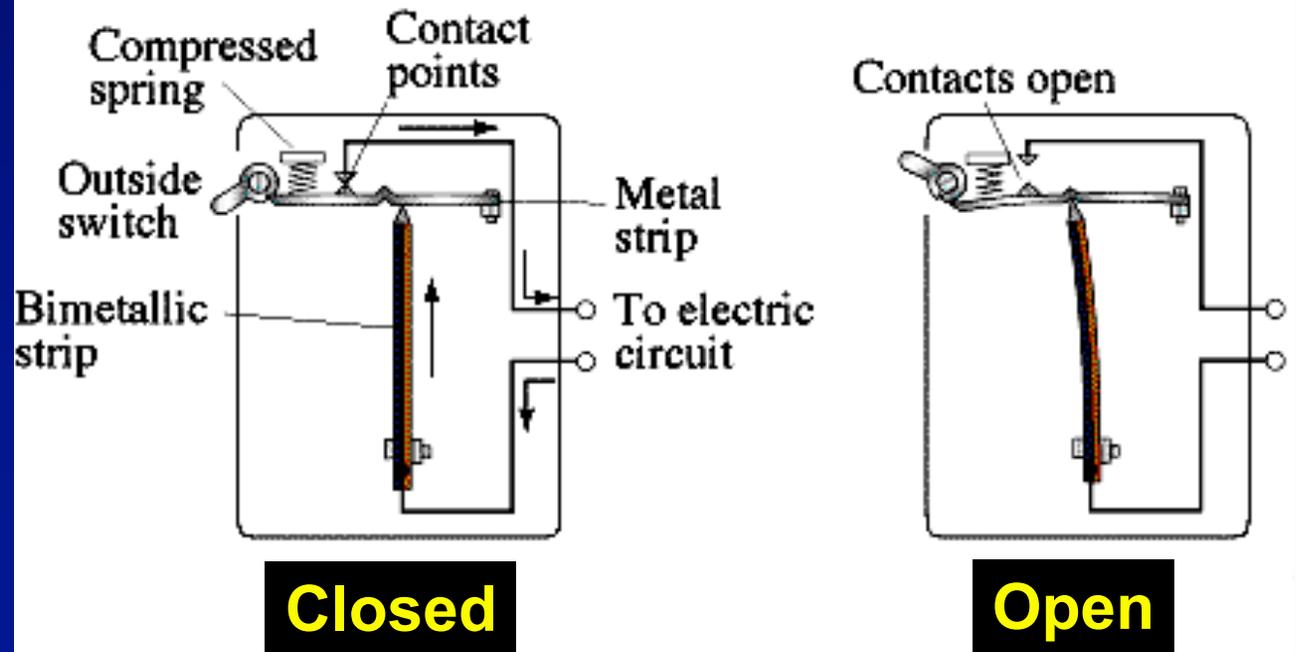

# Power Distribution System

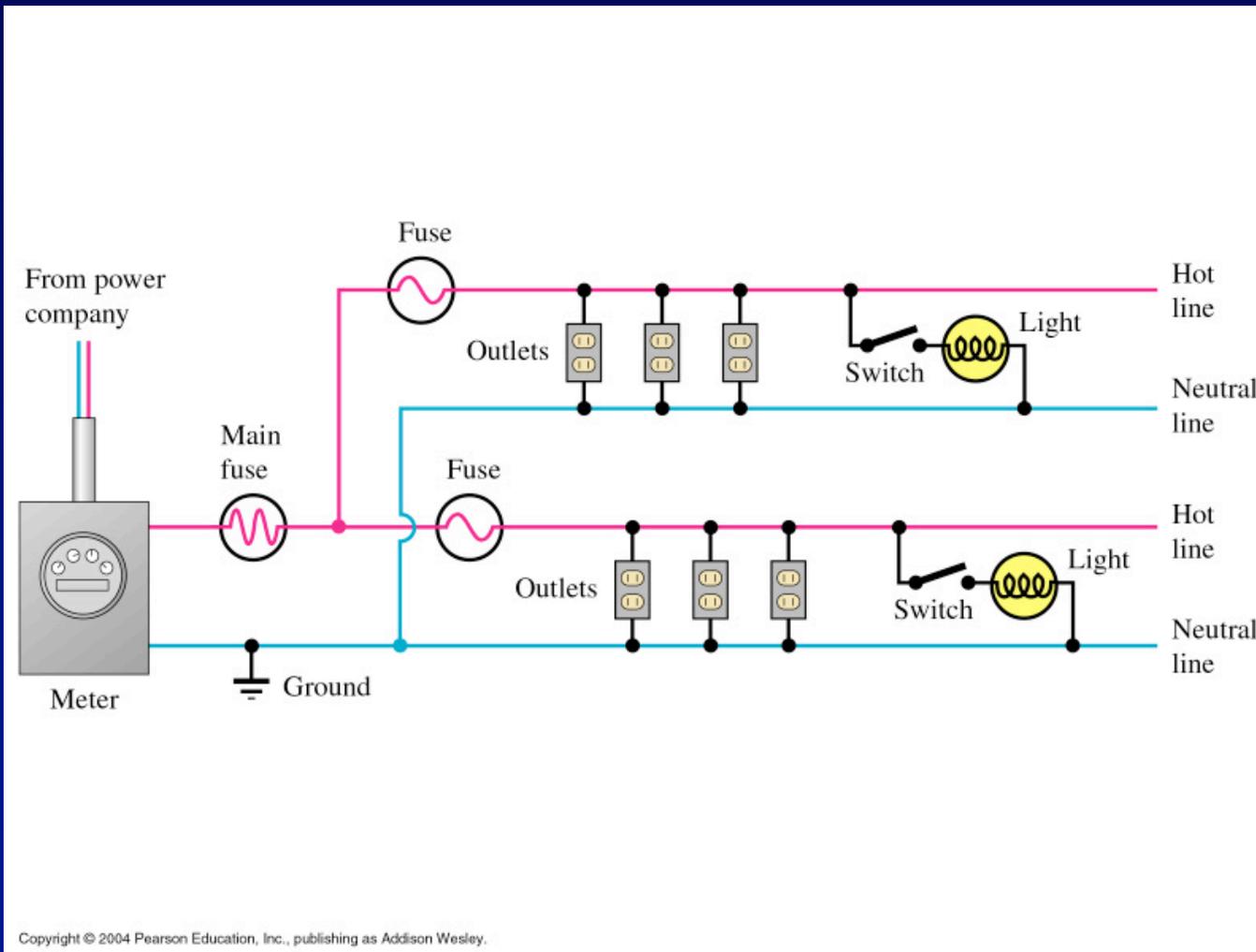

## Example: Will the fuse blow?

- The circuit shown is designed for a **20-A** fuse. Determine the total current drawn by all the devices shown in the circuit.

$$I = P / V$$

$$100/120=0.8 \text{ A}$$

$$1800/120=15 \text{ A}$$

$$350/120=2.9 \text{ A}$$

$$1200/120=10 \text{ A}$$

The total is **28.7 A**.

So it blows if all the devices are used at the same time.

